




Hardware Design Overview

Siddhartha Chowdhury


Secured Embedded Architecture Laboratory (SEAL)
Department of Computer Science and Engineering
Indian Institute of Technology Kharagpur

Bootcamp on Embedded Security and Trust


Digital Design Flow in FPGA

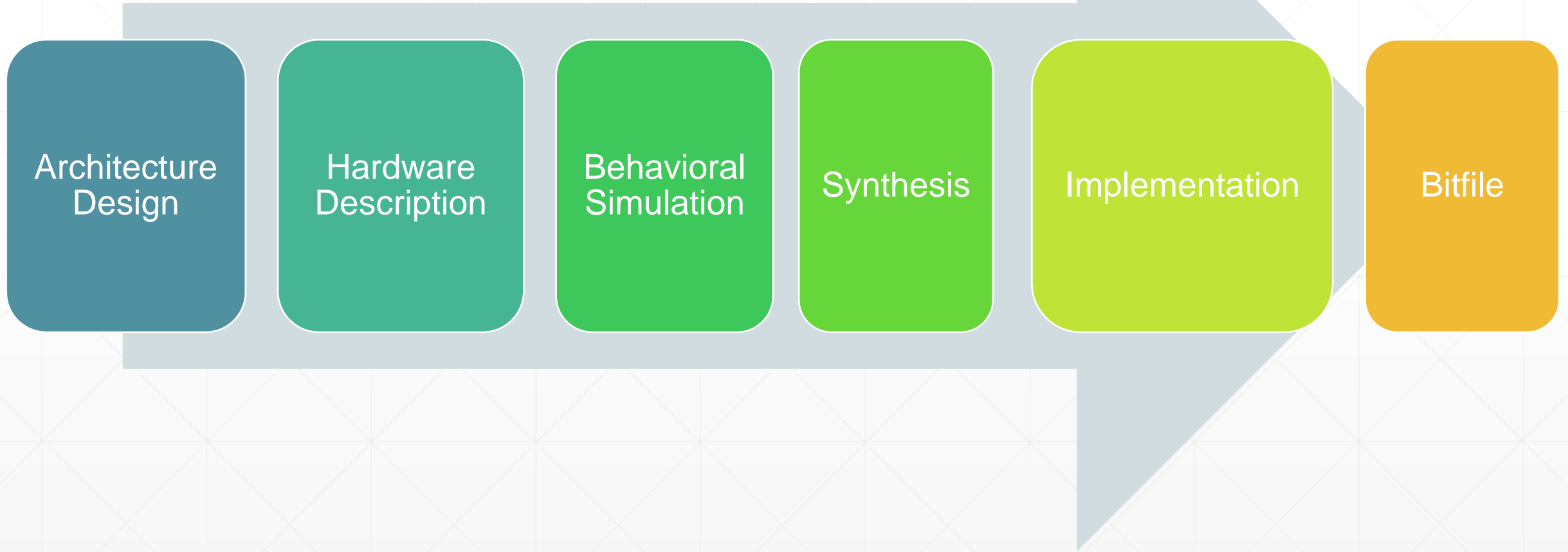


Digital Design Flow in FPGA

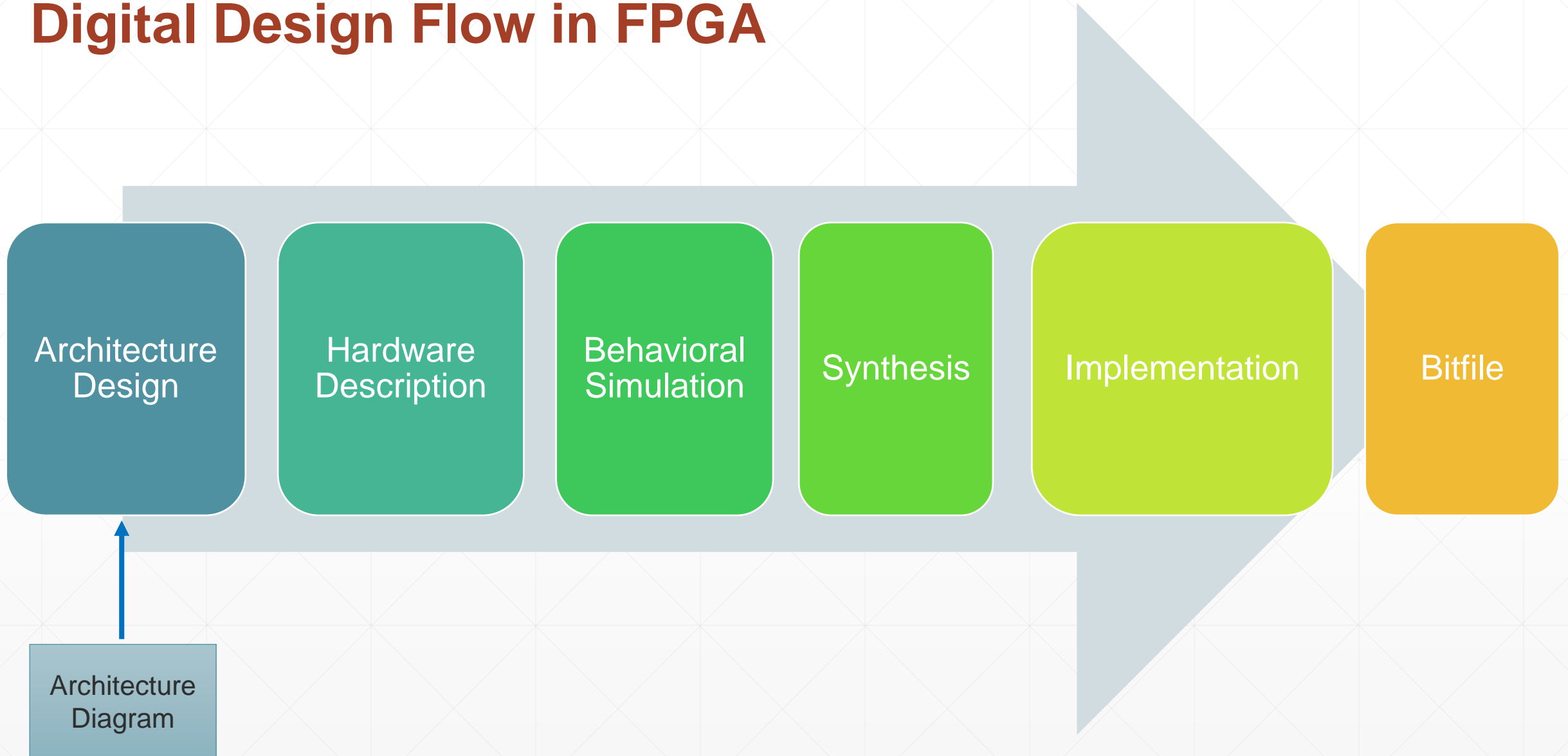


Digital Design Flow in FPGA

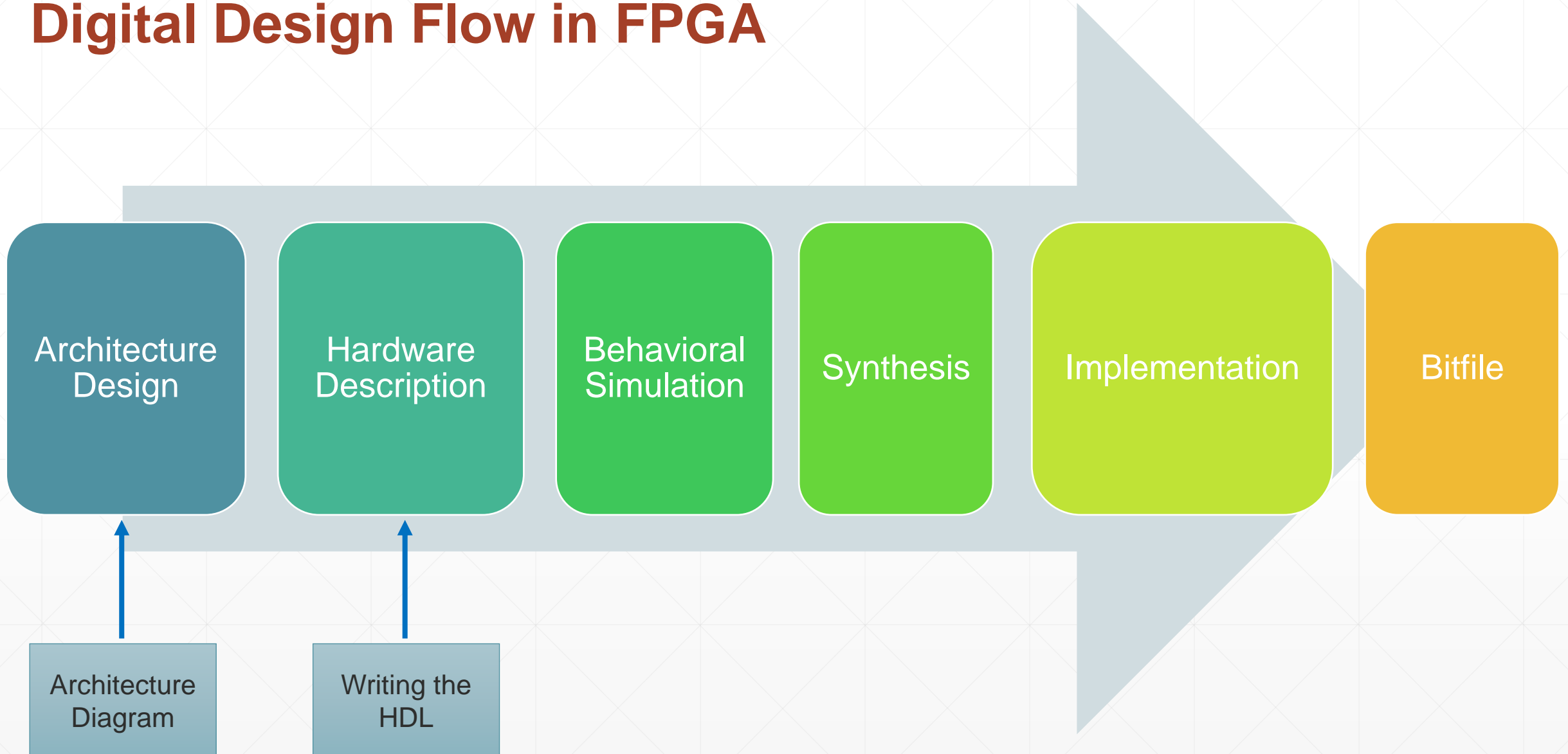


Digital Design Flow in FPGA

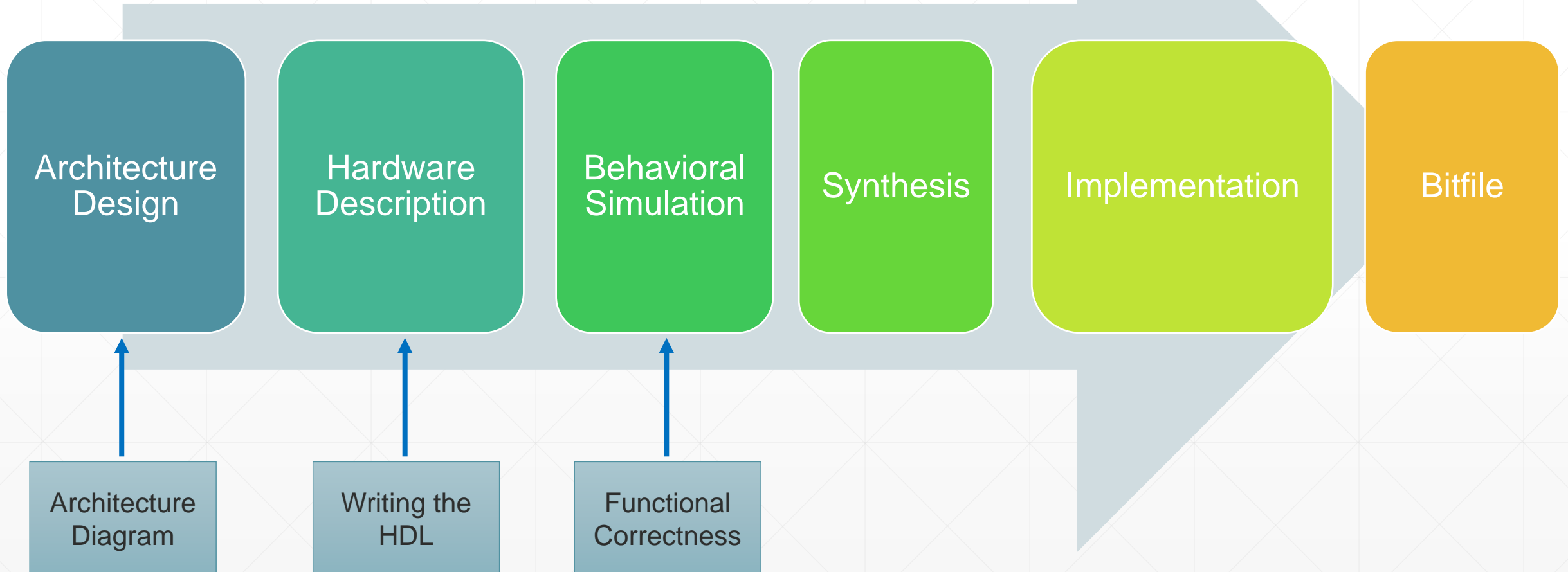


Digital Design Flow in FPGA

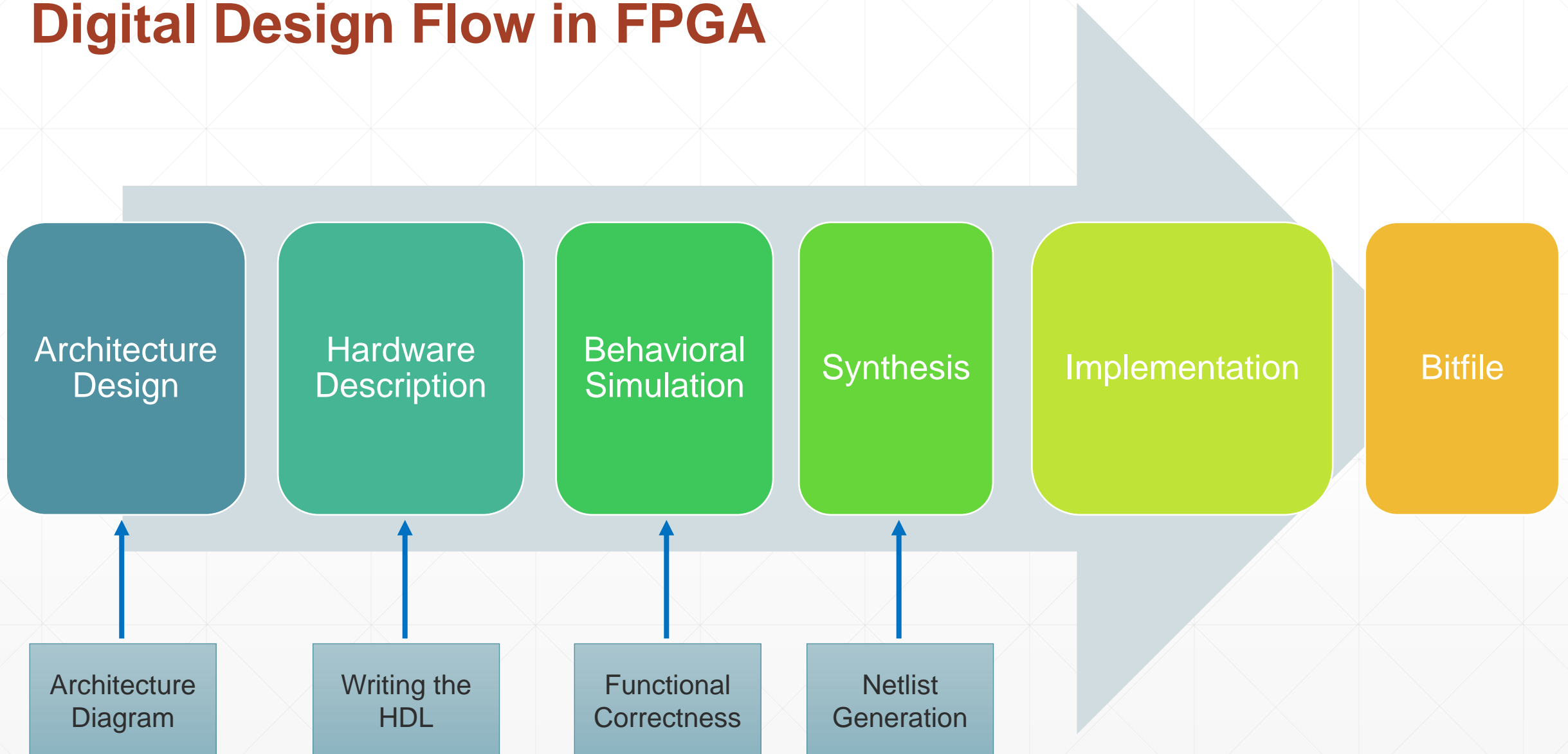


Digital Design Flow in FPGA

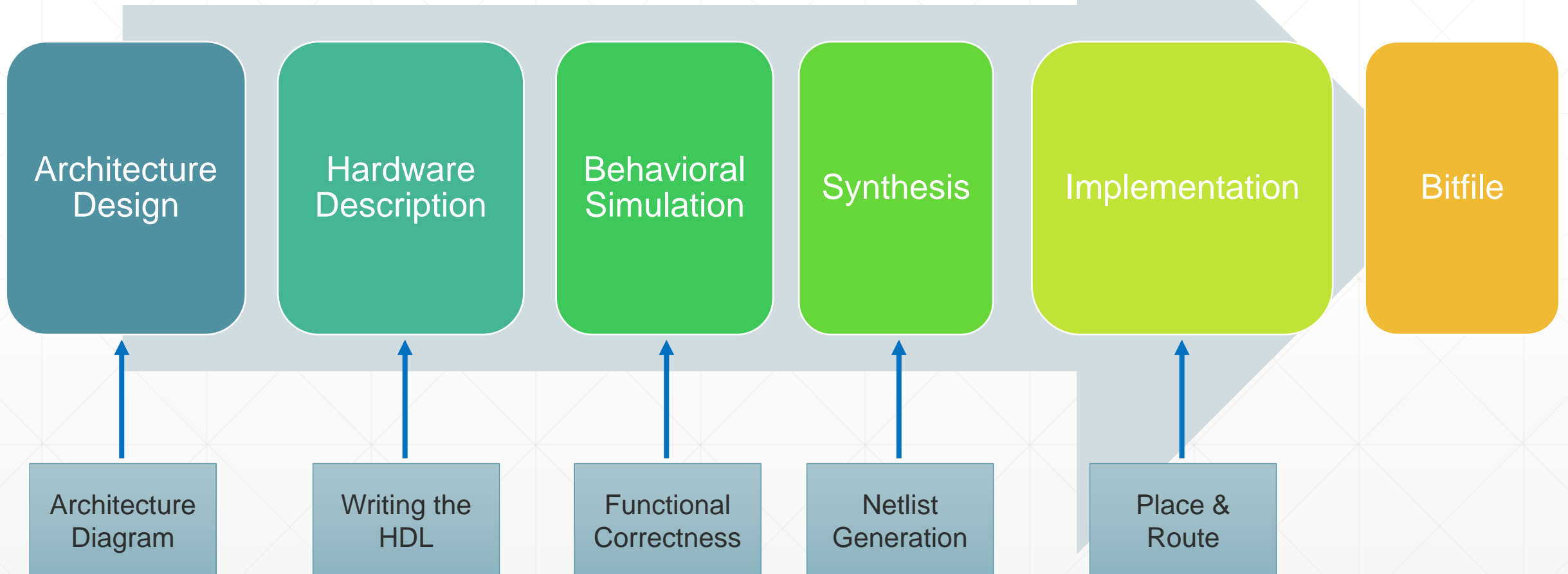


Digital Design Flow in FPGA

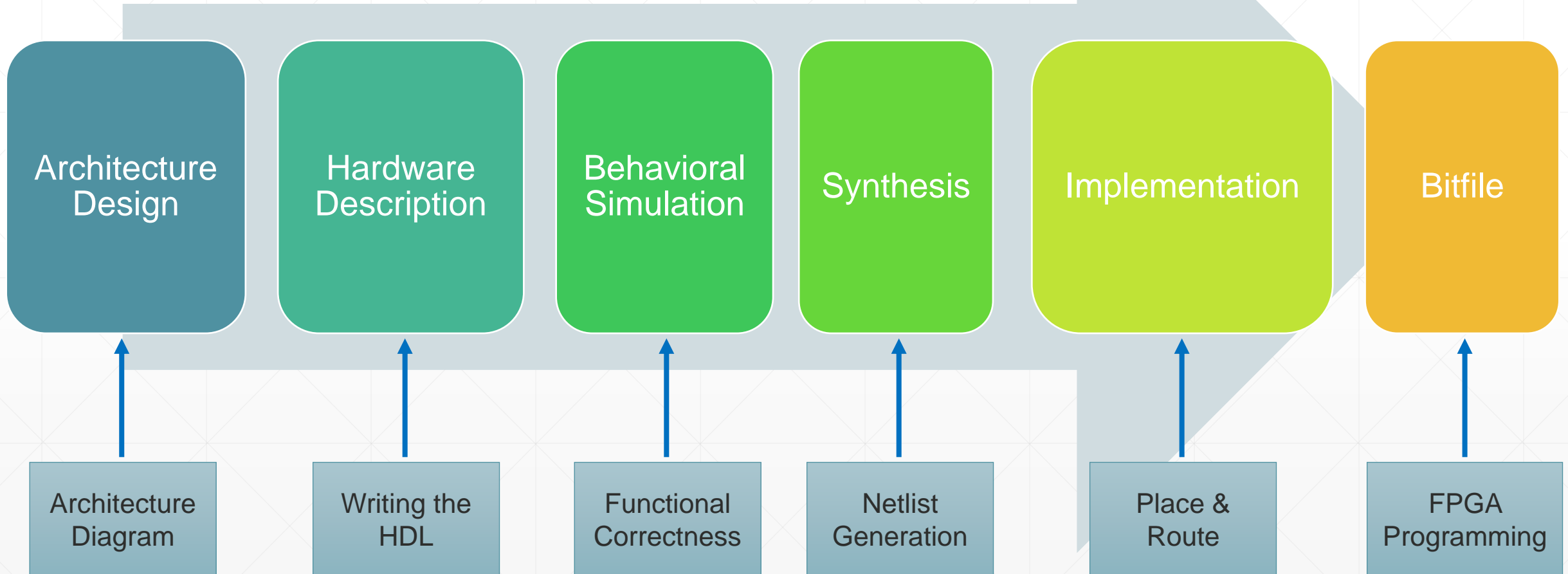

Architecture Design

 

Algorithm

 

Hardware Design Architecture

- Design Datapath Elements
- Design Control Path

Architecture Design


```
# Accumulator Algorithm
accumulator = 0

# Loop for N data inputs
input_data = get_input() # Fetch
new data

accumulator += input_data #
Accumulate (accumulator =
accumulator + input_data)

# Output the final accumulated
value print(accumulator)
```

**Algorithm of the
Accumulator**

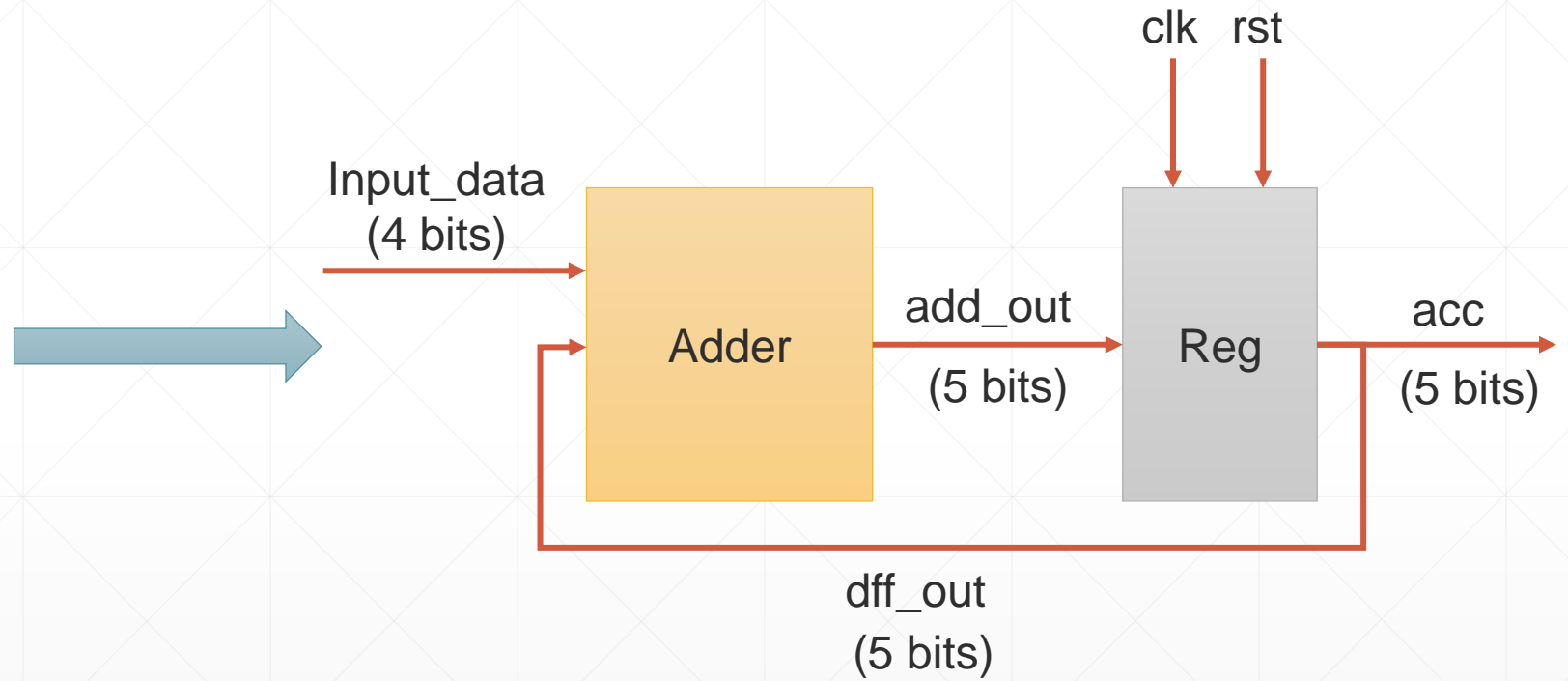

**Hardware Design Architecture of the
Accumulator**

Architecture Design

```
# Accumulator Algorithm
```

```
accumulator = 0
```


```
# Loop for N data inputs
```

```
input_data = get_input() # Fetch  
new data
```

```
accumulator += input_data #  
Accumulate (accumulator =  
accumulator + input_data)
```

```
# Output the final accumulated  
value print(accumulator)
```

Algorithm of the
Accumulator

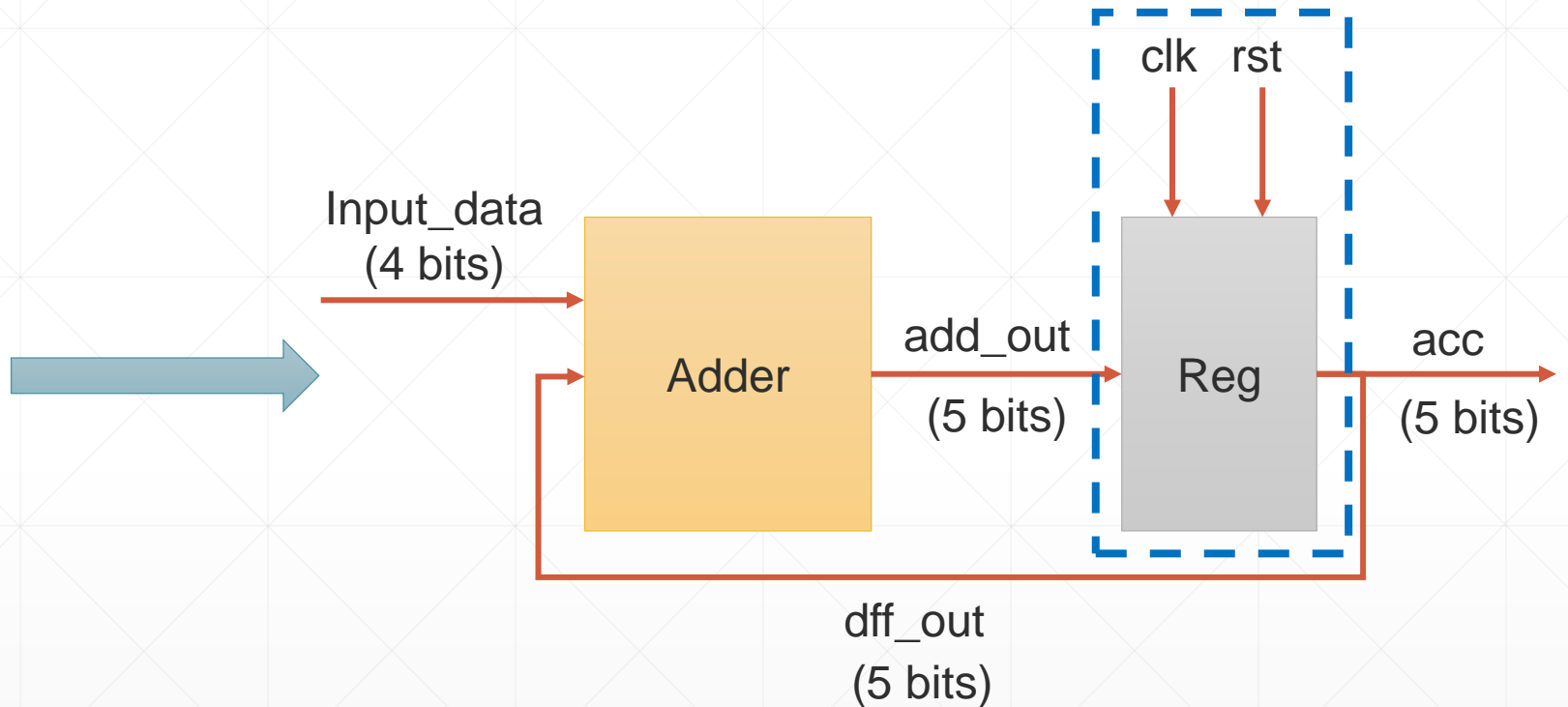

Hardware Design Architecture of the
Accumulator

Architecture Design

```
# Accumulator Algorithm
```

```
accumulator = 0
```


```
# Loop for N data inputs
```

```
input_data = get_input() # Fetch  
new data
```

```
accumulator += input_data #  
Accumulate (accumulator =  
accumulator + input_data)
```

```
# Output the final accumulated  
value print(accumulator)
```

Algorithm of the
Accumulator

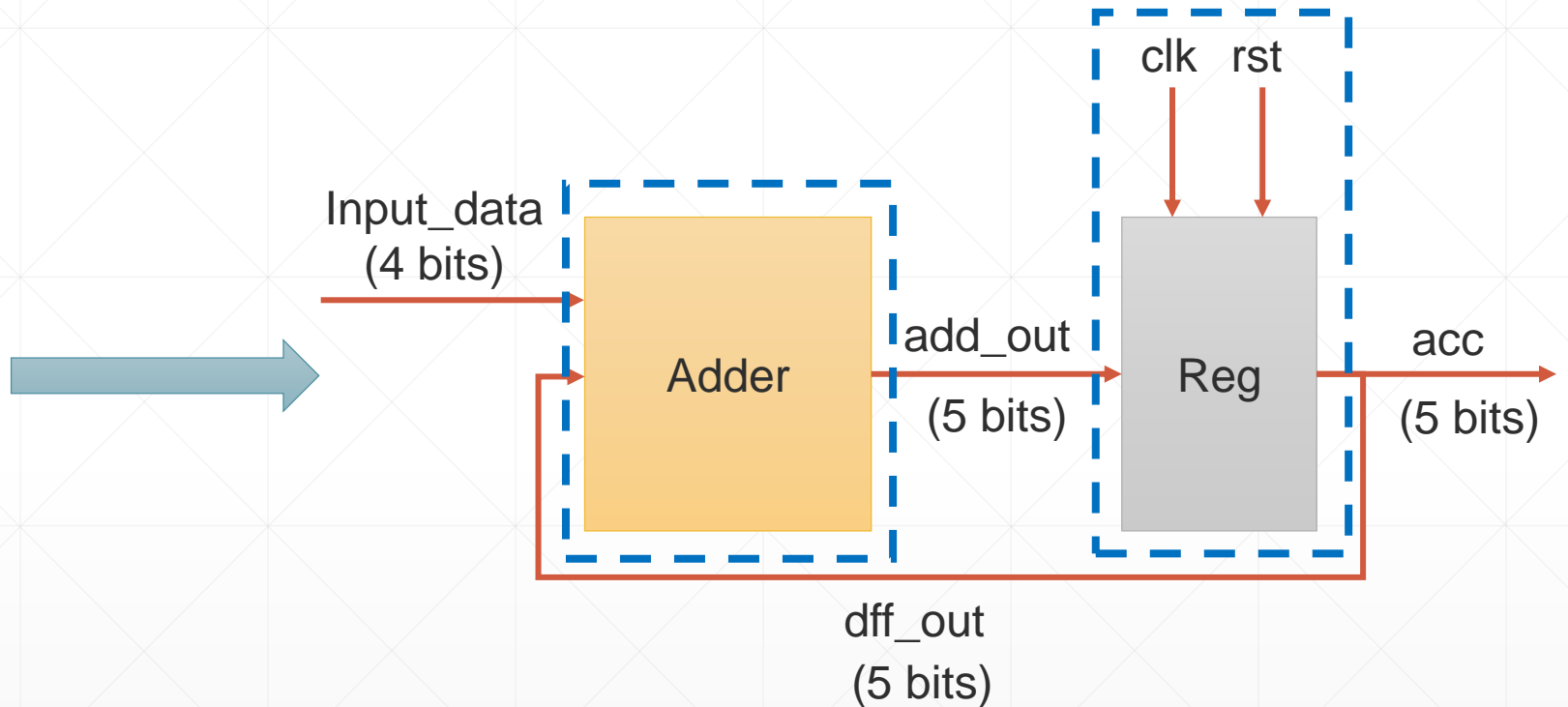

Hardware Design Architecture of the
Accumulator

Architecture Design


```
# Accumulator Algorithm
accumulator = 0

# Loop for N data inputs
input_data = get_input() # Fetch
new data

accumulator += input_data #
Accumulate (accumulator =
accumulator + input_data)


# Output the final accumulated
value print(accumulator)
```

Algorithm of the
Accumulator

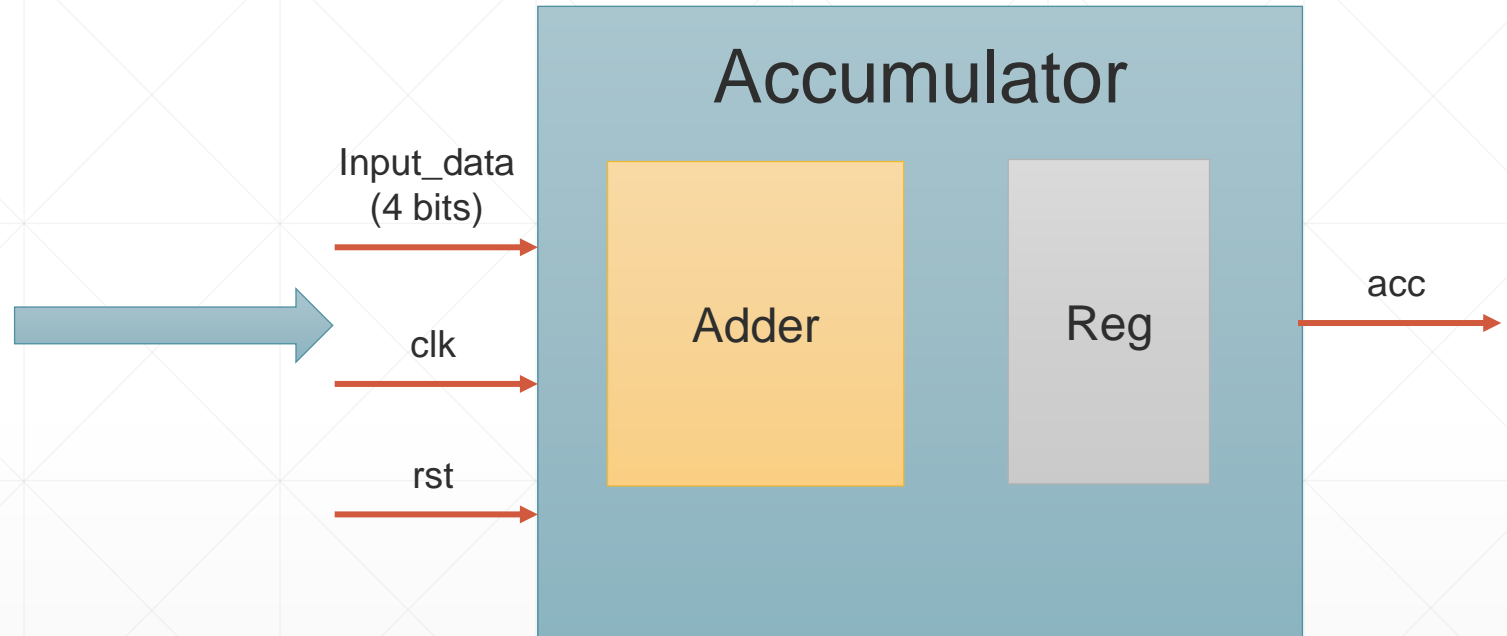


Hardware Design Architecture of the
Accumulator

Datapath Element Design

 


Ripple Carry Adder

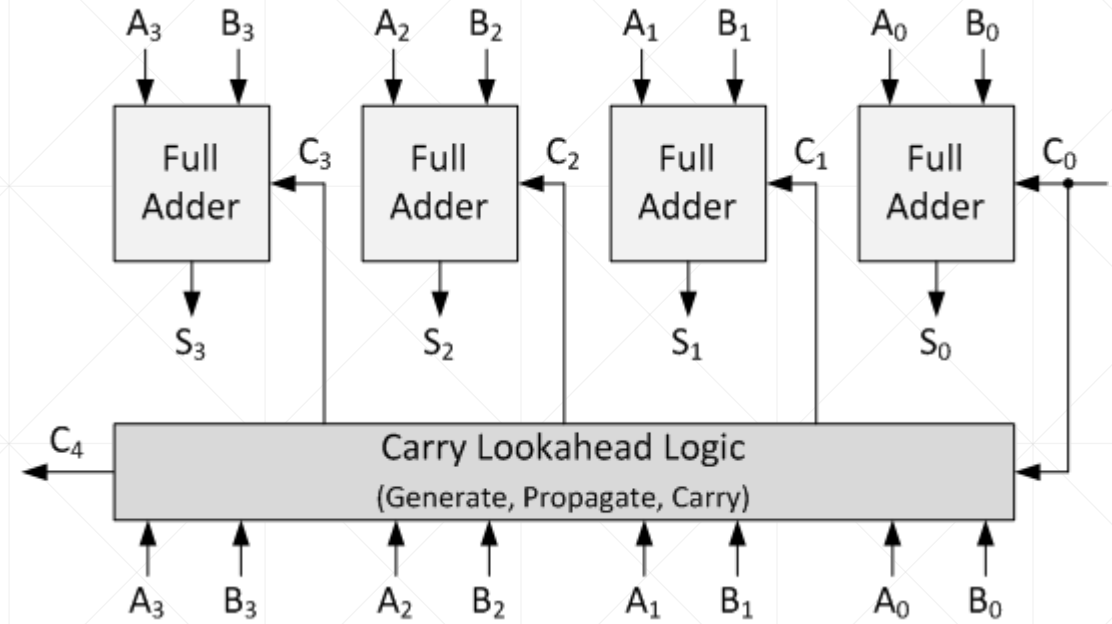

Carry Look Ahead Adder

Datapath Element Design

 


Ripple Carry Adder

Pros:

- Simple design and easy to implement.
- Low area and power consumption for small bit-width adders.

Cons:

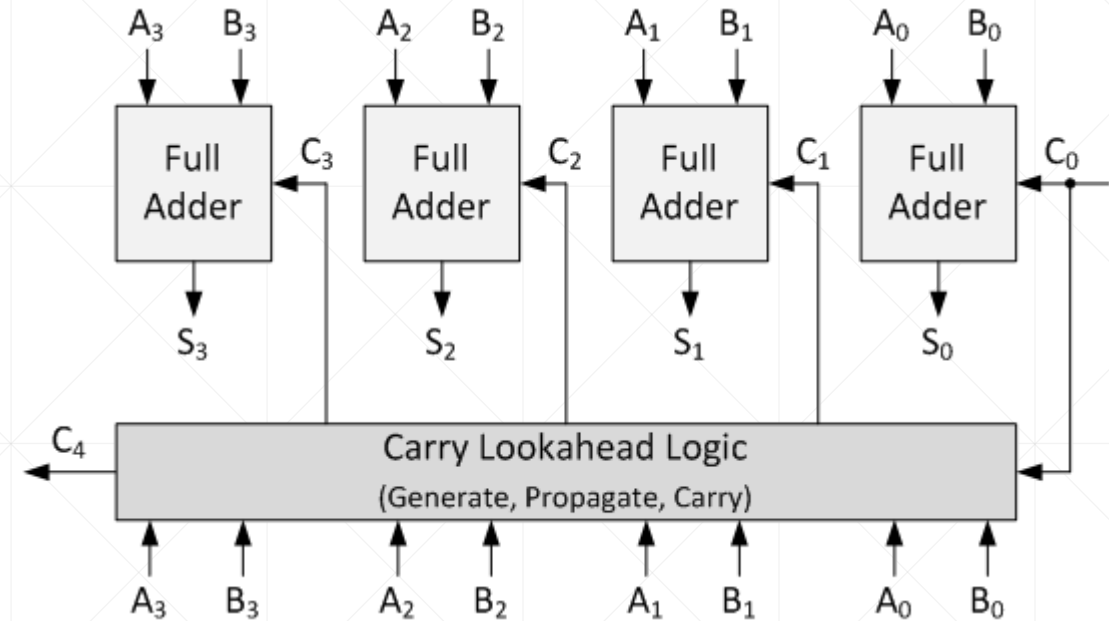- Slow for large bit-widths due to the sequential carry propagation (linear delay).
- Propagation Delay: Increases linearly with the number of bits.



Carry Look Ahead Adder


Pros:

- Much faster than RCA, especially for wide adders.
- Parallel carry computation reduces critical path delay.


Cons:

- More complex design (requires additional logic for generate/propagate).
- Higher area and power consumption due to extra gates.

Datapath Element Design

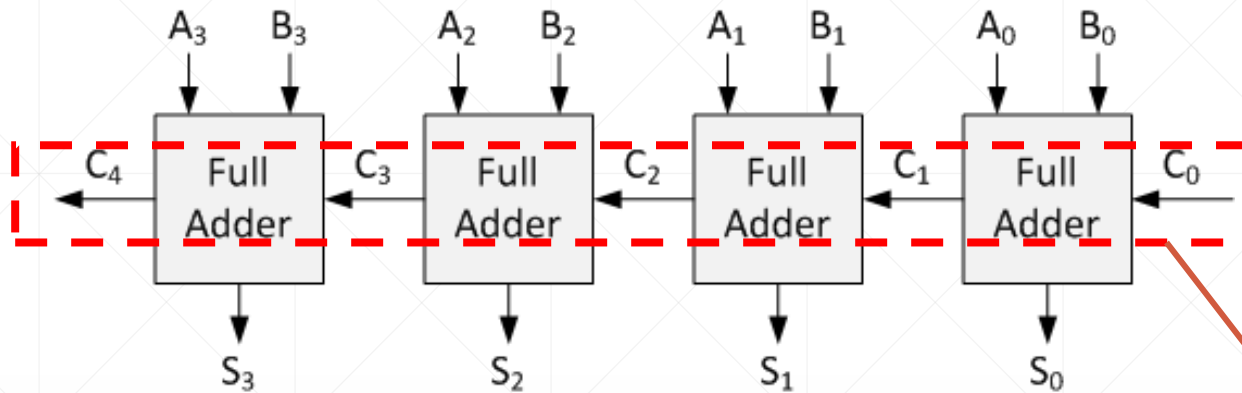

Ripple Carry Adder

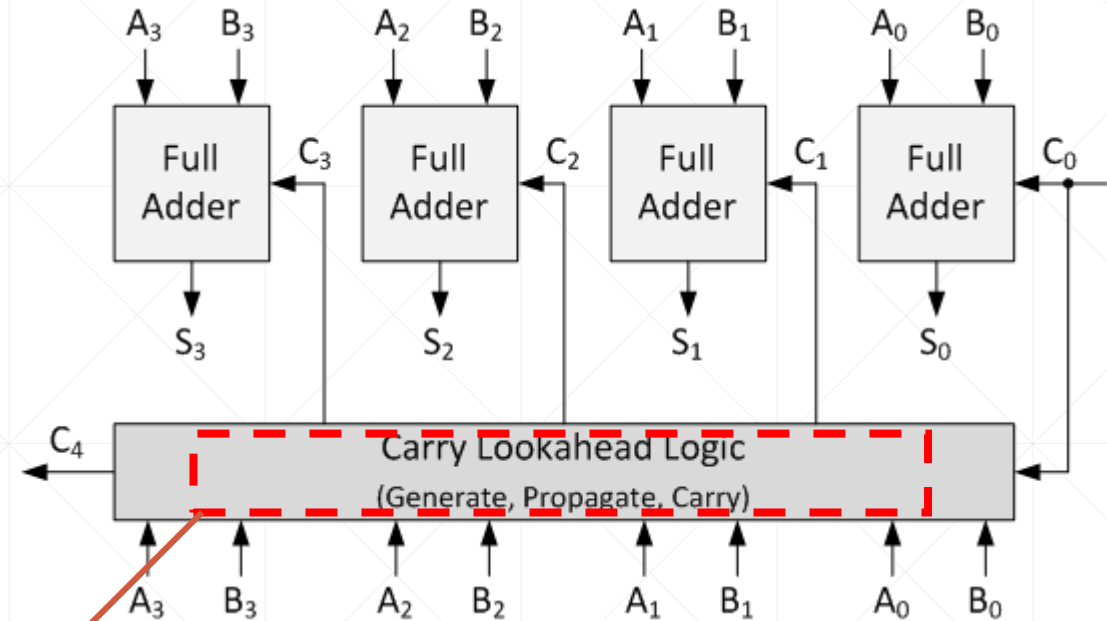

Carry Look Ahead Adder

Pros:

- Simple design and easy to implement.
- Low area and power consumption for small bit-width adders.

Cons:

- Slow for large bit-widths due to the sequential carry propagation (linear delay).
- Propagation Delay: Increases linearly with the number of bits.

Pros:

- Much faster than RCA, especially for wide adders.
- Parallel carry computation reduces critical path delay.

Cons:

- More complex design (requires additional logic for generate/propagate).
- Higher area and power consumption due to extra gates.

Revisit GCD

- **Input:** Integers u and v
- **Output:** Greatest Common Divisor of u and v , $z = \text{gcd}(u, v)$
- while ($u \neq v$) do
 - If (u and v are even)
 - $z = 2 \text{gcd}(u/2, v/2)$
 - else if (u is even and v is odd)
 - $z = \text{gcd}(u/2, v)$
 - else if (u is odd and v is even)
 - $z = \text{gcd}(u, v/2)$

```
else
    if( $u \geq v$ )
         $z = \text{gcd}((u-v)/2, v)$ 
    else
         $z = \text{gcd}(u, (v-u)/2)$ 
```

We need to realize a co-processor on FPGA to compute gcd of two given numbers

References: Hardware Security: Design, Threats, and Safeguards, CRC Press.

Revisit GCD

- **Input:** Integers u and v
- **Output:** Greatest Common Divisor of u and v , $z = \text{gcd}(u, v)$

register u and v

$XR = u$, $YR = v$, $\text{count} = 0$

while ($XR \neq YR$) do

 If ($!XR[0]$ and $!YR[0]$)

$XR = \text{RIGHT_SHIFT}(XR)$

$YR = \text{RIGHT_SHIFT}(YR)$

$\text{Count} = \text{Count} + 1$

 else if ($XR[0]$ and $!YR[0]$)
 $YR = \text{RIGHT_SHIFT}(YR)$
 else if ($!XR[0]$ and $YR[0]$)
 $XR = \text{RIGHT_SHIFT}(XR)$

 else
 if ($XR \geq YR$)
 $XR = \text{RIGHT_SHIFT}(XR - YR)$
 else
 $YR = \text{RIGHT_SHIFT}(YR - XR)$

 while ($\text{count} > 0$)
 $XR = \text{LEFT_SHIFT}(XR)$
 $\text{count} = \text{count} - 1$

References: Hardware Security: Design, Threats, and Safeguards, CRC Press.

Identification of the Data Path Elements

- Subtractor
- Complementer
- Right Shifter
- Left Shifter
- Counter
- Multiplexer:
 - Required in large numbers for the switching necessary for the computations done in the datapath.
 - Selection lines in the multiplexer are configured by the control circuitry, which is essentially a state machine.

References: Hardware Security: Design, Threats, and Safeguards, CRC Press.

Identification of the State Machine of the Control Path

- Control Path is a sequential design.
- It can be represented by a state machine.
- In this example, there are 6 states.
- The controller receives inputs from the partial computations of the datapath.
- Based on the current state and input, it performs state transitions.
- It also produces control signals which configures the datapath elements or switches the multiplexers to sequence the dataflow.

References: Hardware Security: Design, Threats, and Safeguards, CRC Press.

State Machine of the Controller

Present State	Next State					Output Signals										
	0____	100__	110__	101__	111__	<i>load</i> <i>uv</i>	<i>update</i> <i>X_R</i>	<i>update</i> <i>Y_R</i>	<i>load</i> <i>X_R</i>	<i>load</i> <i>Y_R</i>	<i>load_X_R</i> <i>after_sub</i>	<i>load_Y_R</i> <i>after_sub</i>	<i>Update</i> <i>counter</i>	<i>Inc</i> <i>/Dec</i>	<i>left</i> <i>shift</i>	<i>count</i> <i>zero</i>
<i>S</i> ₀	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	1	0	0	1	1	0	0	0	—	—	—
<i>S</i> ₁	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	1	1	1	0	0	1	1	—	—
<i>S</i> ₂	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	0	1	0	1	0	0	0	—	—	—
<i>S</i> ₃	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	0	1	0	0	0	0	—	—	—
<i>S</i> ₄ (<i>X_R</i> ≥ <i>Y_R</i>)	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	0	1	0	1	0	0	—	—	—
<i>S</i> ₄ (<i>X_R</i> < <i>Y_R</i>)	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	0	1	0	1	0	1	0	—	—	—
<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	0	0	0	0	0	0	0	1	0	1	0

There are 6 States of the Controller.

Controller receives 4 inputs from the data-path: [(*X_R* ≠ *Y_R*), *X_R*[0], *Y_R*[0], *X_R* ≥ *Y_R*]

Example:

Present State: *S*₀

load_uv=1, load_XR=load_YR=1.

Input=(0xxx) => *X_R*=*Y_R*=>Next State is *S*₅.

Input=(100x) => *X_R* ≠ *Y_R*, both *X_R* and *Y_R* are even =>Next State is *S*₁.

State Machine of the Controller

Present State	Next State					Output Signals										
	0	100	110	101	111	load _{uv}	update _{X_R}	update _{Y_R}	load _{X_R}	load _{Y_R}	load_X _R _{after_sub}	load_Y _R _{after_sub}	Update _{counter}	Inc/Dec	left_shift	count_zero
S ₀	S ₅	S ₁	S ₂	S ₃	S ₄	1	0	0	1	1	0	0	0	—	—	—
S ₁	S ₅	S ₁	S ₂	S ₃	S ₄	0	1	1	1	1	0	0	1	1	—	—
S ₂	S ₅	S ₁	S ₂	S ₃	S ₄	0	0	1	0	1	0	0	0	—	—	—
S ₃	S ₅	S ₁	S ₂	S ₃	S ₄	0	1	0	1	0	0	0	0	—	—	—
S ₄ (X _R ≥ Y _R)	S ₅	S ₁	S ₂	S ₃	S ₄	0	1	0	1	0	1	0	0	—	—	—
S ₄ (X _R < Y _R)	S ₅	S ₁	S ₂	S ₃	S ₄	0	0	1	0	1	0	1	0	—	—	—
S ₅	S ₅	S ₅	S ₅	S ₅	S ₅	0	0	0	0	0	0	0	1	0	1	0

There are 6 States of the Controller.

Controller receives 4 inputs from the data-path: **$[(XR \neq YR), XR[0], YR[0], XR \geq YR]$**

Example:

Present State: S_0

$load_{uv}=1, load_{XR}=load_{YR}=1.$

Input=(0xxx) $\Rightarrow XR=YR \Rightarrow$ Next State is S_5 .

Input=(100x) $\Rightarrow XR \neq YR$, both XR and YR are even \Rightarrow Next State is S_1 .

State Machine of the Controller

Present State	Next State					Output Signals										
	0____	100__	110__	101__	111__	<i>load</i> <i>uv</i>	<i>update</i> <i>X_R</i>	<i>update</i> <i>Y_R</i>	<i>load</i> <i>X_R</i>	<i>load</i> <i>Y_R</i>	<i>load_X_R</i> <i>after_sub</i>	<i>load_Y_R</i> <i>after_sub</i>	<i>Update</i> <i>counter</i>	<i>Inc</i> <i>/Dec</i>	<i>left</i> <i>shift</i>	<i>count</i> <i>zero</i>
<i>S</i> ₀	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	1	0	0	1	1	0	0	0	—	—	—
<i>S</i> ₁	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	1	1	1	0	0	1	1	—	—
<i>S</i> ₂	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	0	1	0	1	0	0	0	—	—	—
<i>S</i> ₃	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	0	1	0	0	0	0	—	—	—
<i>S</i> ₄ (<i>X_R</i> ≥ <i>Y_R</i>)	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	1	0	1	0	1	0	0	—	—	—
<i>S</i> ₄ (<i>X_R</i> < <i>Y_R</i>)	<i>S</i> ₅	<i>S</i> ₁	<i>S</i> ₂	<i>S</i> ₃	<i>S</i> ₄	0	0	1	0	1	0	1	0	—	—	—
<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	<i>S</i> ₅	0	0	0	0	0	0	0	1	0	1	0

Present State: S1


load_uv=0, load_XR=load_YR=1, update_XR=update_YR=1, Update Counter=1, Inc/Dec=1.

Input=(0xxx)=>XR=YR=>Next State is S5.

Input=(100x)=>XR!=YR, both XR and YR are even=>Next State is S1.

Input=(110x)=>XR!=YR, XR is odd, YR is even=>Next State is S2.

State Machine of the Controller

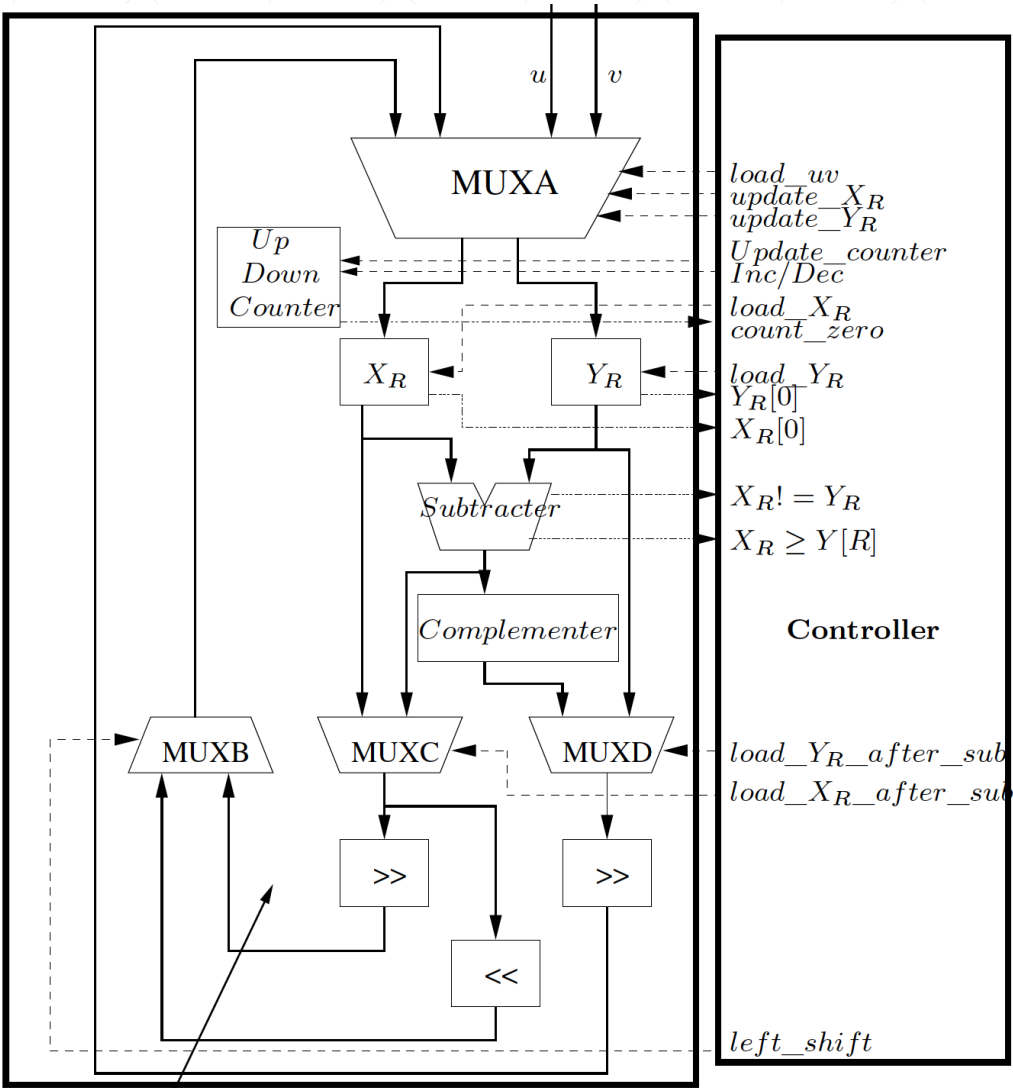

1

State Initialization and State Transition

2


Next State Logic

3

Control Signal Logic at Present State

Data path comprising of computational and switching elements

State Machine of the Controller

 


```

always @(posedge clk)
begin
    if(reset)
        state<=S0;
    else
        state<=next_state;
    end
endmodule
    
```

Data path comprising of computational and switching elements

State Machine of the Controller

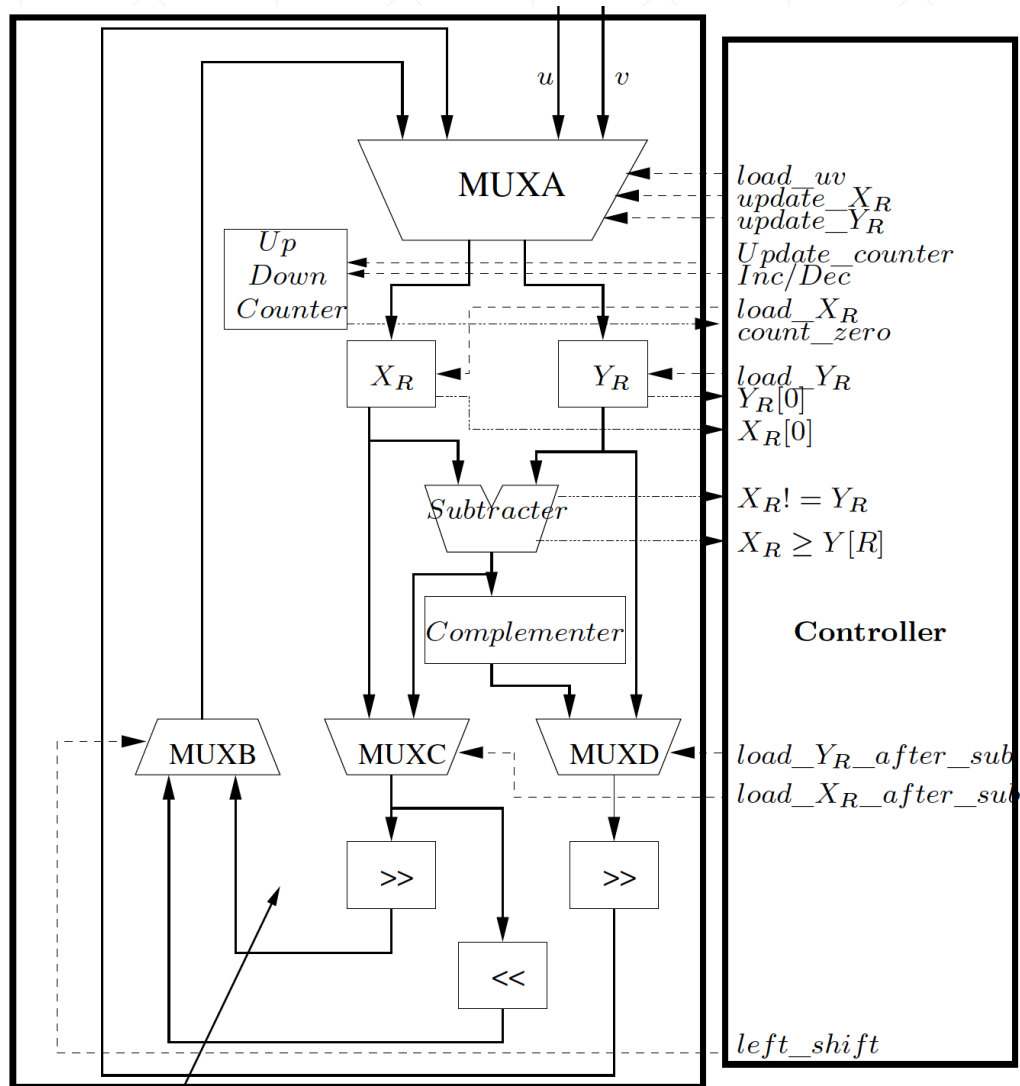


Data path comprising of computational and switching elements

```

localparam S0 = 3'd0;
localparam S1 = 3'd1;
localparam S2 = 3'd2;
localparam S3 = 3'd3;
localparam S4 = 3'd4;
localparam S5 = 3'd5;
always @(state or in)
begin
    if(!in[0])
        next_state <= S5;
    else if(in[0] && in[3]==0 && in[2]==0)
        next_state <= S1;
    else if(in[0] && in[3]==1 && in[2]==0)
        next_state <= S2;
    else if(in[0] && in[3]==0 && in[2]==1)
        next_state <= S3;
    else if(in[0] && in[3]==1 && in[2]==1)
        next_state <= S4;
    else if(state == S5)
        next_state <= S5;
    else
        next_state <= S0;
    if(state == S5)
        next_state <= S5;
end
    
```

State Machine of the Controller

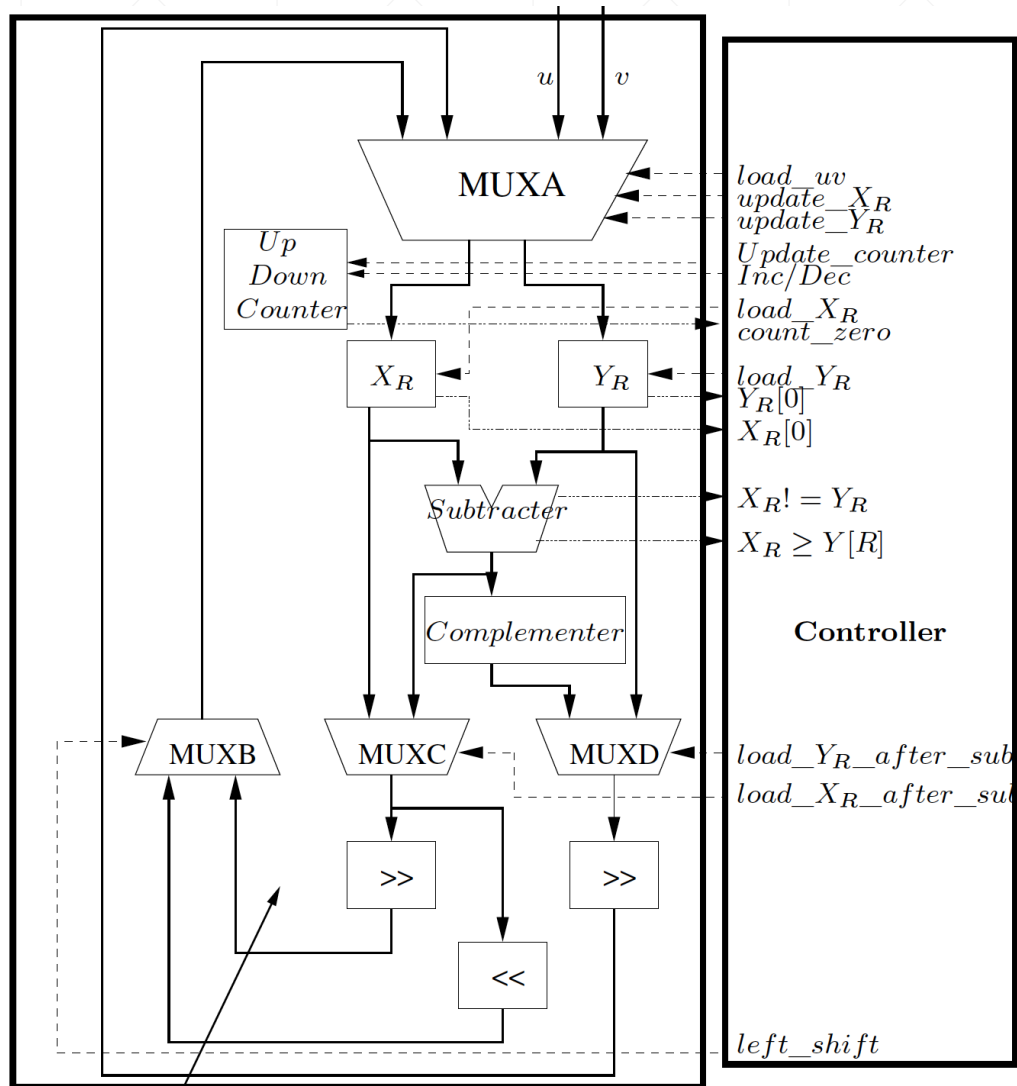

Data path comprising of computational and switching elements

```
always @(state or in or done or cnt_zero)
begin
```

```
case(state)
```

```
S0:
```

```
begin
```

```
ld_in1_in2<=1;
```

```
update_Xr<=0;
```

```
update_Yr<=0;
```

```
ld_Xr<=1;
```

```
ld_Yr<=1;
```

```
ld_Xr_aftr_subs<=0;
```

```
ld_Yr_aftr_subs<=0;
```

```
lShift<=0;
```

```
end
```

```
S1:
```

```
begin
```

```
ld_in1_in2<=0;
```

```
update_Xr<=1;
```

```
update_Yr<=1;
```

```
update_Counter<=1;
```

```
incr_dec<=1;
```

```
ld_Xr<=1;
```

```
ld_Yr<=1;
```

```
ld_Xr_aftr_subs<=0;
```

```
ld_Yr_aftr_subs<=0;
```

```
lShift<=0;
```

```
end
```

```
S2:
```

```
begin
```

```
ld_in1_in2<=0;
```

```
update_Xr<=0;
```

```
update_Yr<=1;
```

```
update_Counter<=0;
```

```
incr_dec<=0;
```

```
ld_Xr<=0;
```

```
ld_Yr<=1;
```

```
ld_Xr_aftr_subs<=0;
```

```
ld_Yr_aftr_subs<=0;
```

```
lShift<=0;
```

```
end
```

```
S3:
```

```
begin
```

```
ld_in1_in2<=0;
```

```
update_Xr<=1;
```

```
update_Yr<=0;
```

```
update_Counter<=0;
```

```
incr_dec<=0;
```

```
ld_Xr<=1;
```

```
ld_Yr<=0;
```


```
ld_Xr_aftr_subs<=0;
```

```
ld_Yr_aftr_subs<=0;
```

```
lShift<=0;
```

```
end
```


Lookup Tables

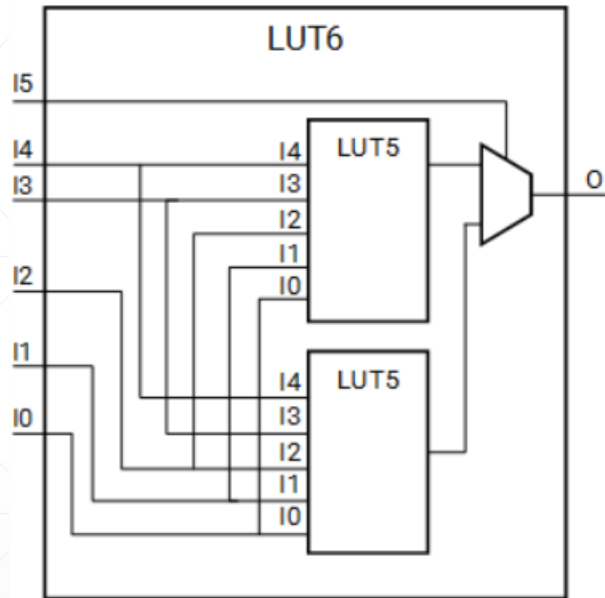

**6-Input Look-Up Table with
General Output**

6-input, 1-output look-up table (LUT) that can either act as an asynchronous 64-bit ROM (with 6-bit addressing) or implement any 6-input logic function.

Lookup Tables

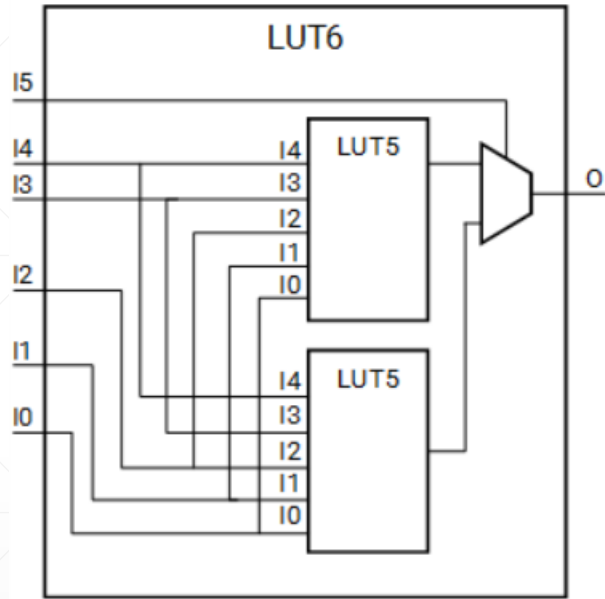


**6-Input Look-Up Table with
General Output**

6-input, 1-output look-up table (LUT) that can either act as an asynchronous 64-bit ROM (with 6-bit addressing) or implement any 6-input logic function.

SRAM Cells: Each bit in a LUT is stored in a small SRAM cell that holds either a '0' or a '1'.

The LUT acts like a simple **multiplexer (MUX)**, selecting the output based on the current input combination. The stored SRAM bits are the MUX's inputs.

Lookup Tables

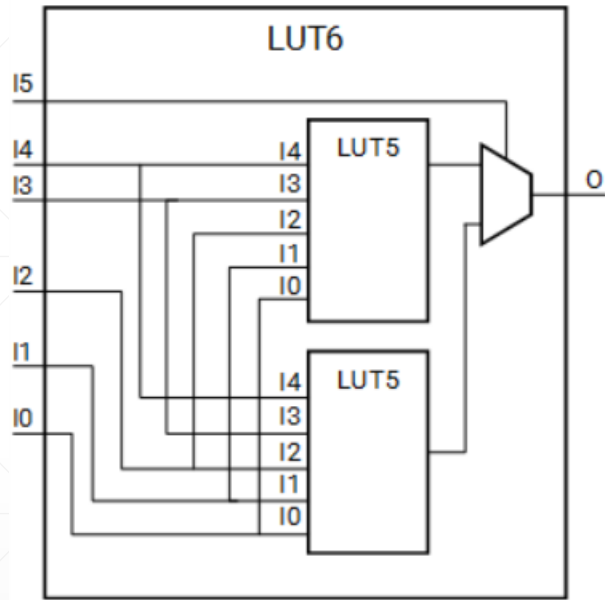

6-Input Look-Up Table with General Output


6-input, 1-output look-up table (LUT) that can either act as an asynchronous 64-bit ROM (with 6-bit addressing) or implement any 6-input logic function.

SRAM Cells: Each bit in a LUT is stored in a small SRAM cell that holds either a '0' or a '1'.



The LUT acts like a simple **multiplexer (MUX)**, selecting the output based on the current input combination. The stored SRAM bits are the MUX's inputs.

Some FPGAs allow LUTs to be used as small RAMs (**LUTRAM**), where dynamic data can be written during operation.

AES Algorithm

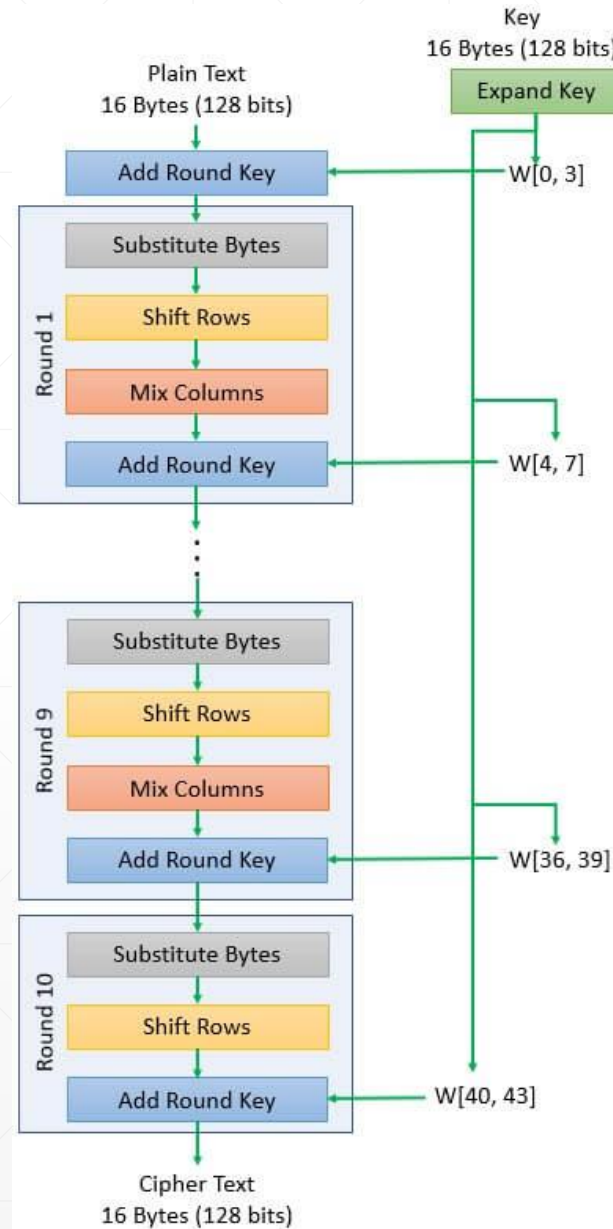

Sub Byte Operation

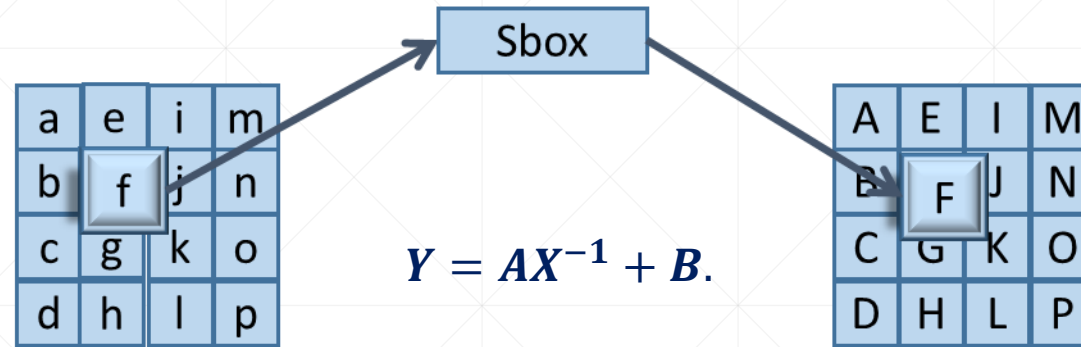 

```
module sbox(a,c);
```

```
input [7:0] a;
output [7:0] c;
```

```
reg [7:0] c;
```

```
always @(a)
```

```
case (a)
```

```
8'h00: c=8'h63;
```

```
8'h01: c=8'h7c;
```

```
8'h02: c=8'h77;
```



```
8'h03: c=8'h7b;
```

```
8'h04: c=8'hf2;
```

```
8'h05: c=8'h6b;
```

```
8'h06: c=8'h6f;
```


Sub Byte Operation

 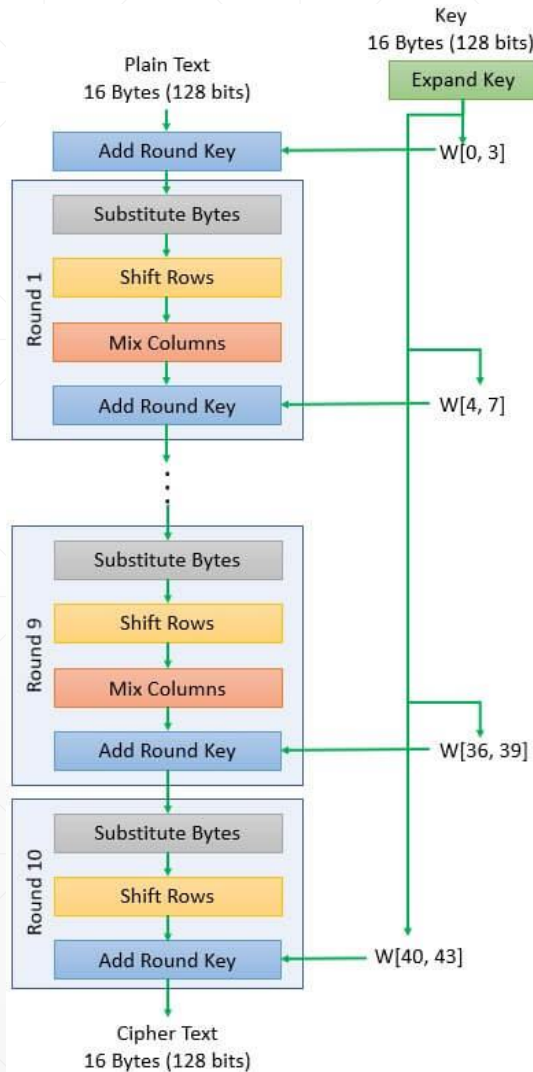

```

module sbox(input[7:0] sboxIn,output[7:0] sboxOut);
wire[7:0] inverterOut,Aout;

inverter invMod(sboxIn,inverterOut);


A_mult Amod(inverterOut,Aout);

assign sboxOut[7]=Aout[7];
assign sboxOut[6]=Aout[6]^1'b1;
assign sboxOut[5]=Aout[5]^1'b1;
assign sboxOut[4]=Aout[4];
assign sboxOut[3]=Aout[3];
assign sboxOut[2]=Aout[2];
assign sboxOut[1]=Aout[1]^1'b1;
assign sboxOut[0]=Aout[0]^1'b1;

endmodule

```

Shift Row Operation

 

a	e	i	m
b	f	j	n
c	g	k	o
d	h	l	p



k ₀	k ₄	k ₈	k ₁₂
k ₁	k ₅	k ₉	k ₁₃
k ₂	k ₆	k ₁₀	k ₁₄
k ₃	k ₇	k ₁₁	k ₁₅



a + k ₀	e + k ₄	i + k ₈	m + k ₁₂
b + k ₁	f + k ₅	j + k ₉	n + k ₁₃
c + k ₂	g + k ₆	k + k ₁₀	o + k ₁₄
d + k ₃	h + k ₇	l + k ₁₁	p + k ₁₅

```

assign sr[127:120] = sb[127:120];
assign sr[119:112] = sb[87:80];
assign sr[111:104] = sb[47:40];
assign sr[103:96] = sb[7:0];

```

```

assign sr[95:88] = sb[95:88];
assign sr[87:80] = sb[55:48];
assign sr[79:72] = sb[15:8];
assign sr[71:64] = sb[103:96];

```

```

assign sr[63:56] = sb[63:56];
assign sr[55:48] = sb[23:16];
assign sr[47:40] = sb[111:104];
assign sr[39:32] = sb[71:64];



```

```

assign sr[31:24] = sb[31:24];
assign sr[23:16] = sb[119:112];
assign sr[15:8] = sb[79:72];
assign sr[7:0] = sb[39:32];

```


Mix Column Operation

  


```

function [7:0] mixcolumn32;
input [7:0] i1,i2,i3,i4;
begin
mixcolumn32[7]=i1[6] ^ i2[6] ^ i2[7] ^ i3[7] ^ i4[7];
mixcolumn32[6]=i1[5] ^ i2[5] ^ i2[6] ^ i3[6] ^ i4[6];
mixcolumn32[5]=i1[4] ^ i2[4] ^ i2[5] ^ i3[5] ^ i4[5];
mixcolumn32[4]=i1[3] ^ i1[7] ^ i2[3] ^ i2[4] ^ i2[7] ^ i3[4] ^ i4[4];
mixcolumn32[3]=i1[2] ^ i1[7] ^ i2[2] ^ i2[3] ^ i2[7] ^ i3[3] ^ i4[3];
mixcolumn32[2]=i1[1] ^ i2[1] ^ i2[2] ^ i3[2] ^ i4[2];
mixcolumn32[1]=i1[0] ^ i1[7] ^ i2[0] ^ i2[1] ^ i2[7] ^ i3[1] ^ i4[1];
mixcolumn32[0]=i1[7] ^ i2[7] ^ i2[0] ^ i3[0] ^ i4[0];
end
endfunction
    
```


AES Hardware

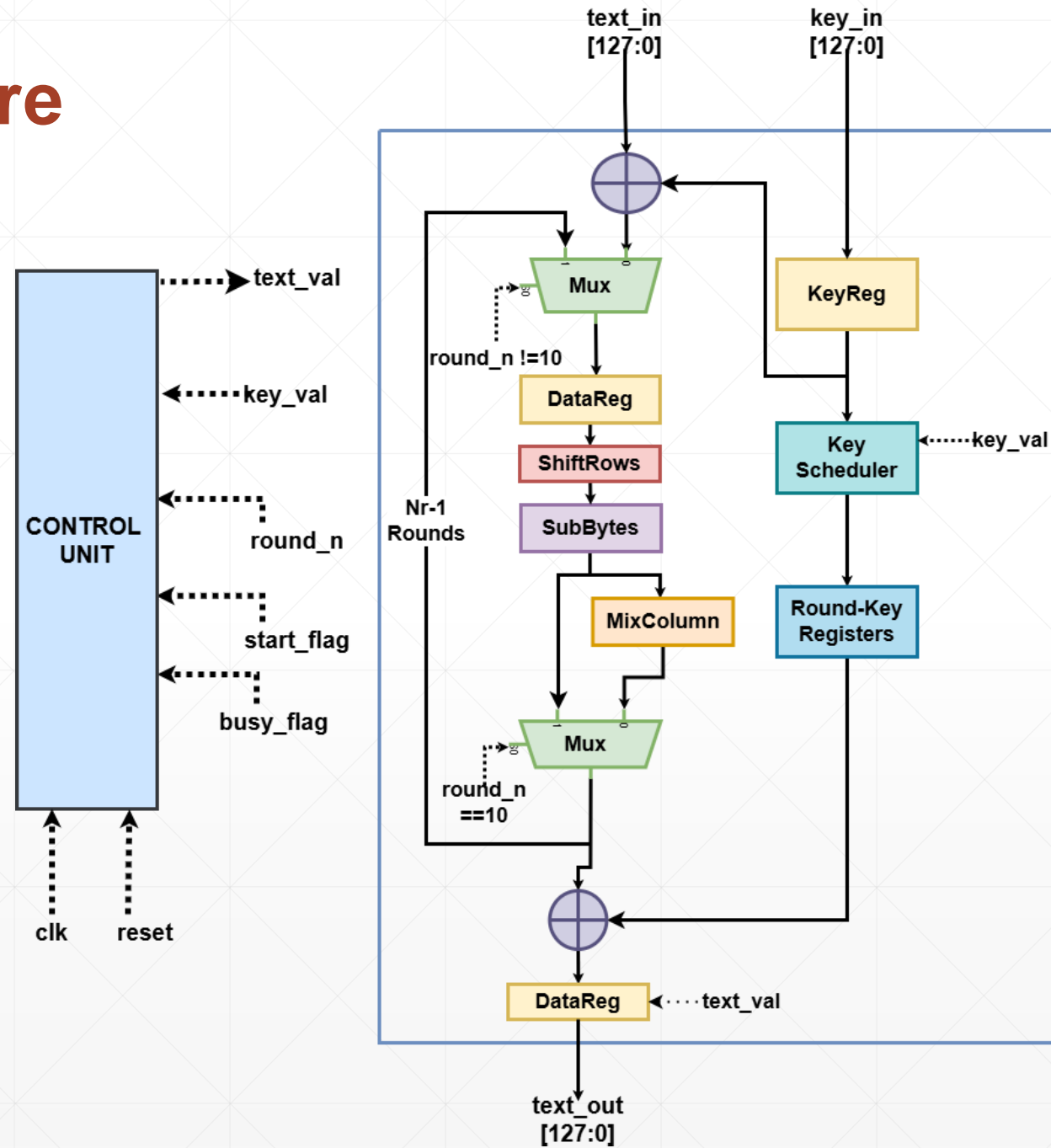


AES Hardware

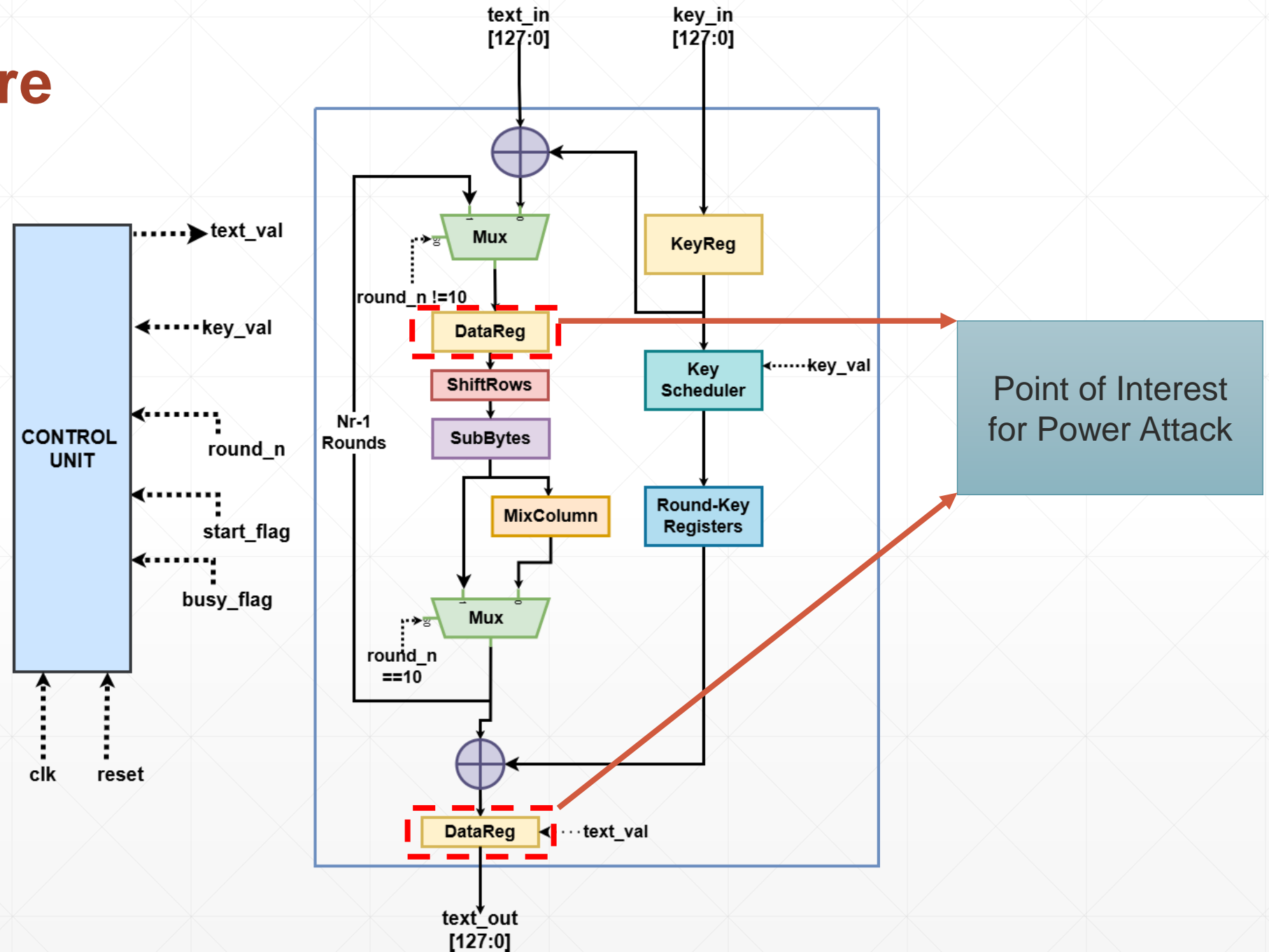

Digital Design Flow in FPGA

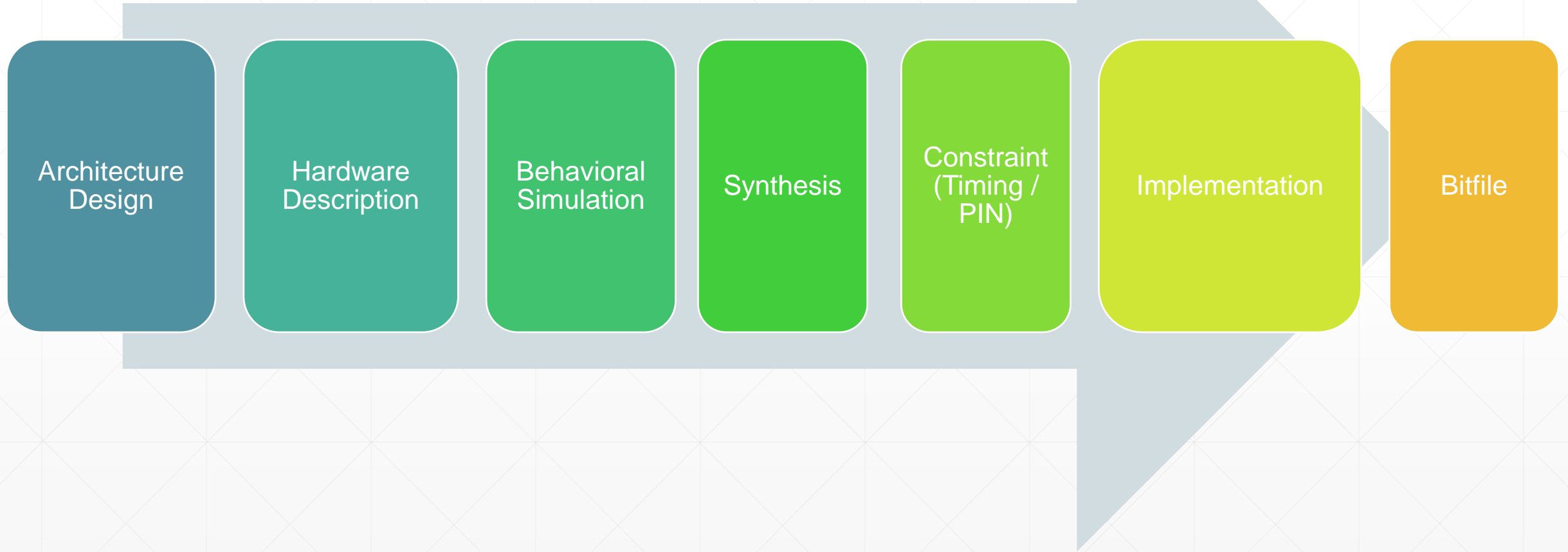

Digital Design Flow in FPGA

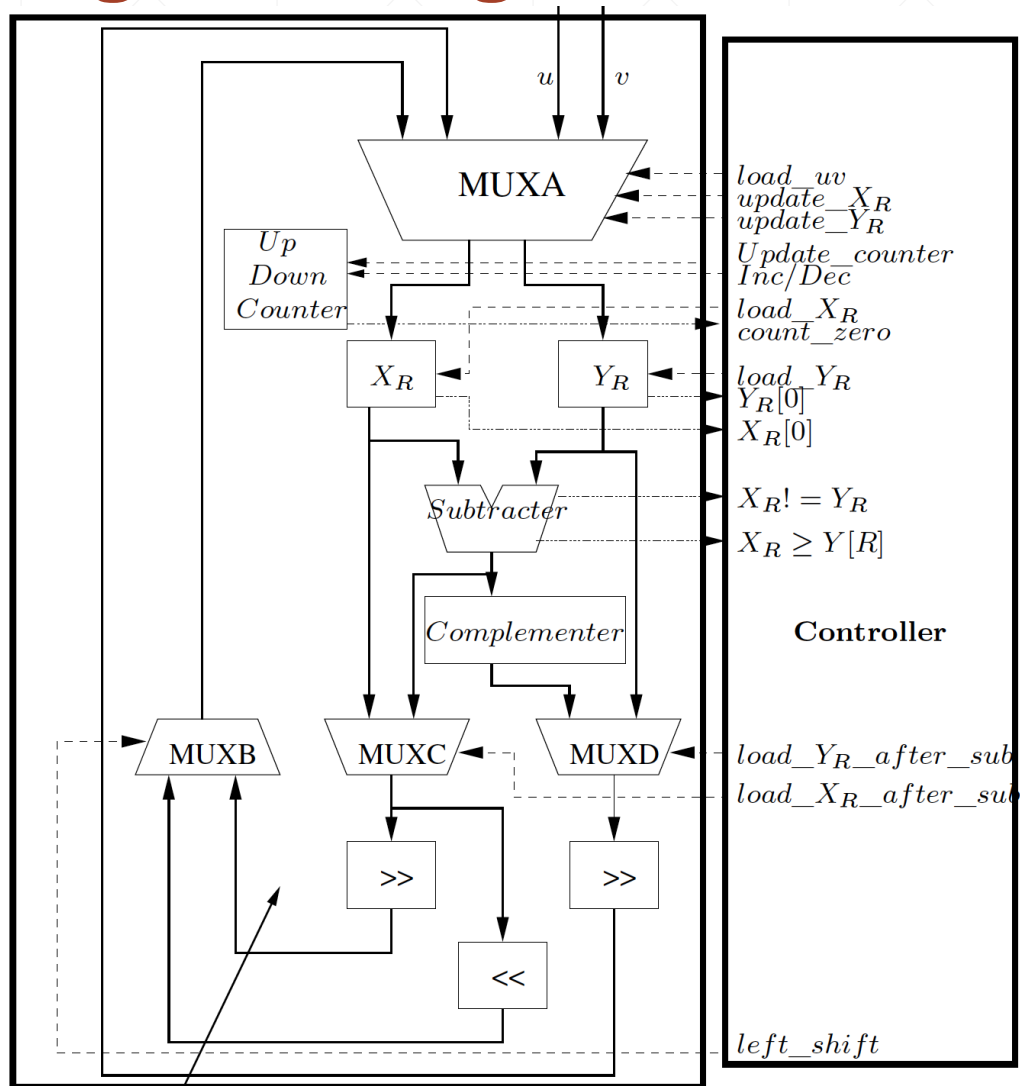


Data path comprising of computational and switching elements

```

module gcd
#(parameter WIDTH =32) // Bit
width
(
input[WIDTH-1:0] in1,
input[WIDTH-1:0] in2,
input clk,
input reset,
output reg[WIDTH-1:0] out,
output reg done
);
    
```

Digital Design Flow in FPGA

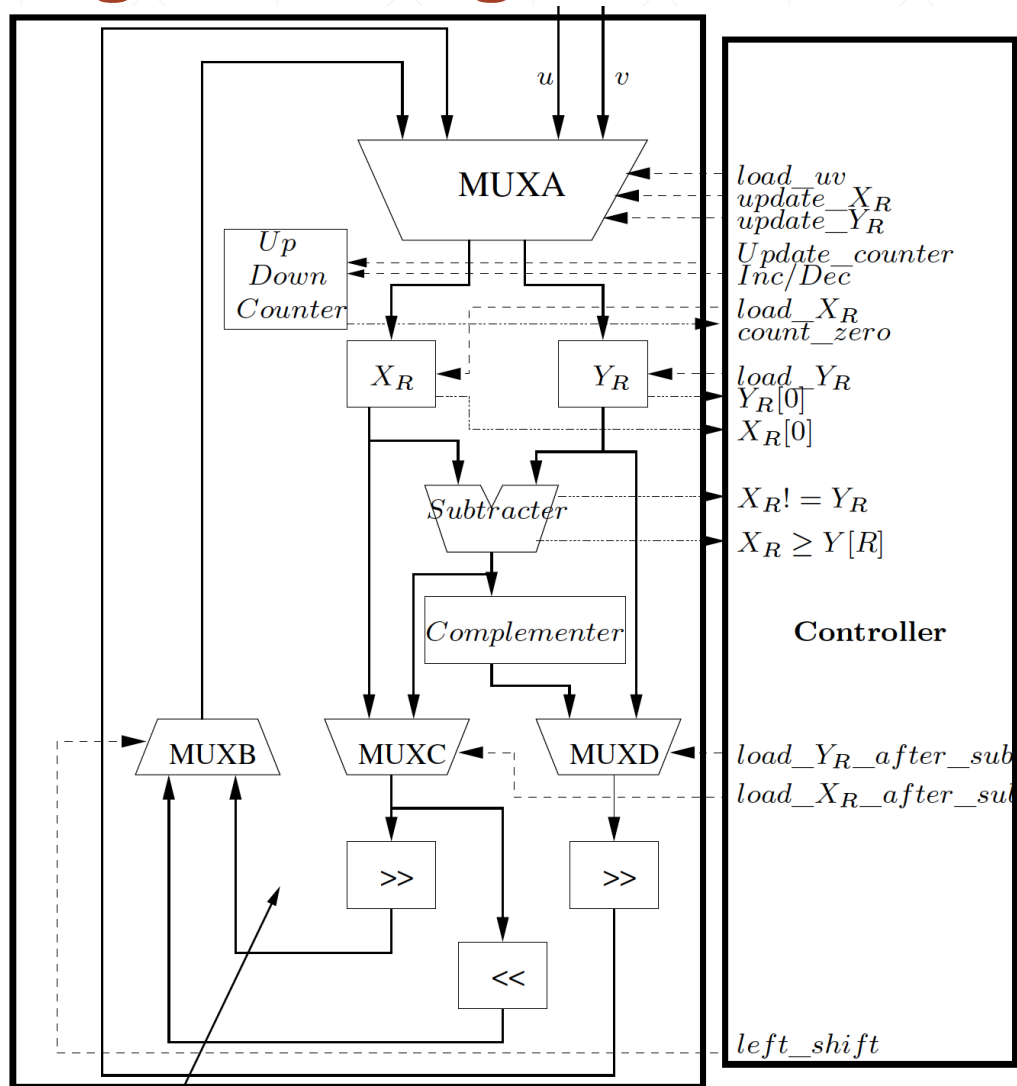

Data path comprising of computational and switching elements

```

module gcd
#(parameter WIDTH =32) // Bit
width
(
input[WIDTH-1:0] in1,
input[WIDTH-1:0] in2,
input clk,
input reset,
output reg[WIDTH-1:0] out,
output reg done
);
    
```

```

create_clock -period 2.2 -name clk -
waveform {0.000 1.1} [get_ports {clk}]
    
```


Thank You